


New Scheme




**GOVERNMENT OF KARNATAKA
KARNATAKA STATE PRE-UNIVERSITY EDUCATION EXAMINATION BOARD
II YEAR PUC EXAMINATION**




SCHEME OF VALUATION March 2017

Subject code: 40(NS)

Subject: Electronics

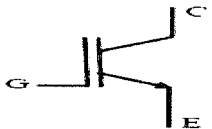Qn No	Part-A		Marks
1	Source supplies charge carriers for the conduction		1
2	Class- A Power amplifier.		1
3	It is the rate of change of output voltage with time.		1
4	5 KHz		1
5	The process of recovering original modulating signal from modulated wave.		1
6			1
7	A logic circuit used for counting the pulses.		1
8	$(1011)_G$		1
9	6 including RESET OR 5 excluding RESET.		1
10	$\text{Sqrt}(a \cdot a + b \cdot b)$.		1
Part-B			
11		FET	BJT
	1	It is unipolar device	It is bipolar device
	2	It is voltage controlled device	It is current controlled device
	3	Input resistance is very high	Input resistance is very low
	4	It has high switching speed	It has low switching speed
	5	Less noise	High noise
	6	Current conduction is due to majority charge carriers	Current conduction is due to both majority and minority charge carriers
(any two)			
12	Remove all ac sources, open all capacitors, short all inductors if any.		2
13		Positive feedback	Negative feedback
	1	Feedback signal is in phase with input signal	Feedback signal is out of phase with input signal
	2	Used in oscillators	Used in amplifiers
	3	Gain is high or gain increases	Gain is low or gain decreases
	4	Frequency band width low	Frequency band width high
(any two)			

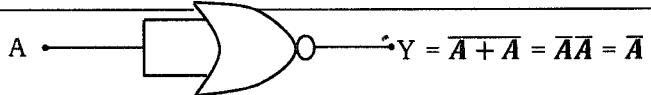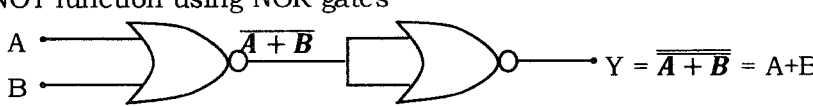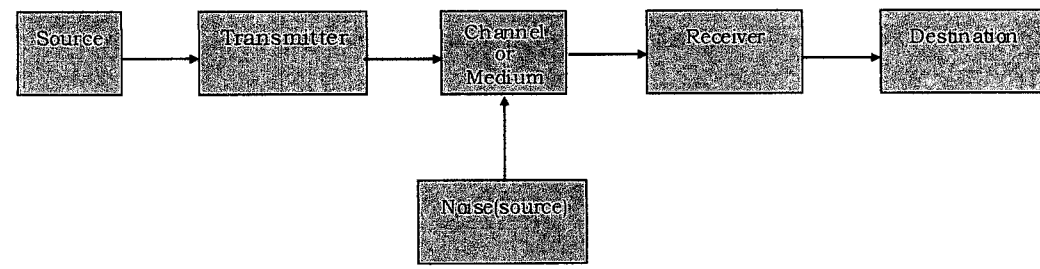14	RC Oscillators do not require inductors, hence size of the circuit and cost are reduced. Provide constant output and good stability.	1 1									
15	$I = I_s \left[e^{\frac{qV}{kT}} - 1 \right]$ where I _s - reverse saturation current, K-Boltzman constant, I-Current through diode, T-Temperature in Kelvin, q- Charge of electron, V-voltage across diode.	1									
15	Duty ratio=T _{on} /T =0.5mS/2mS=0.25 V _{dc} =Duty ratio*V _s =0.25*24=6v	1 1									
17	 <p>NOT function using NOR gates</p>  <p>OR function using NOR gates</p>	1 1									
18	<table border="1" style="width:100%; border-collapse: collapse;"> <thead> <tr> <th style="width:5%;"></th> <th style="width:45%;">Uplink signal</th> <th style="width:45%;">Downlink Signal</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>Signal transmitted from ground station to satellite</td> <td>Signal transmitted from satellite to ground station on earth</td> </tr> <tr> <td>2</td> <td>Frequency range is 6GHz</td> <td>Frequency range is 4GHz</td> </tr> </tbody> </table>		Uplink signal	Downlink Signal	1	Signal transmitted from ground station to satellite	Signal transmitted from satellite to ground station on earth	2	Frequency range is 6GHz	Frequency range is 4GHz	1 1
	Uplink signal	Downlink Signal									
1	Signal transmitted from ground station to satellite	Signal transmitted from satellite to ground station on earth									
2	Frequency range is 6GHz	Frequency range is 4GHz									
Part-C											
19	A straight line which joins saturation point and cutoff point on output characteristics of transistor is called DC load line Q point does not shift , Provide excellent stabilization and Provide better amplification (any two points)	1 2									
20	$Z_{if} = Z_i (1+A\beta)$ $= 10 \times 10^3 (1 + 100 \times 0.01)$ $= 20K\Omega$	1 1 1									
21	 <p style="text-align: center;">Basic communication system</p> <p>Brief explanation of each block</p>	1 2									

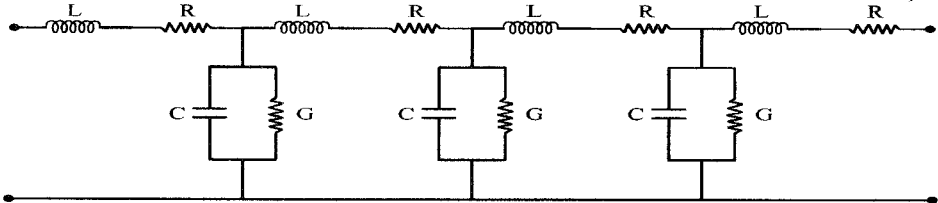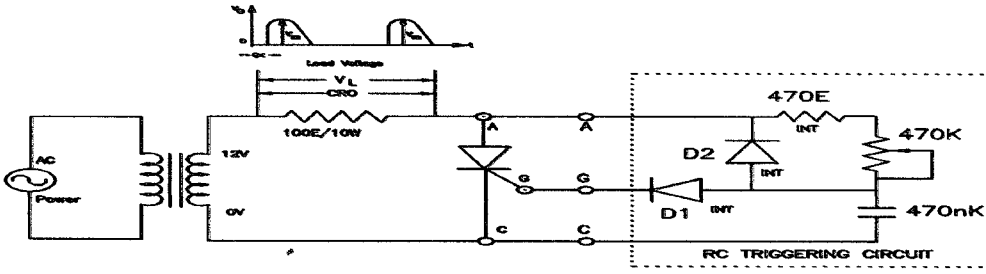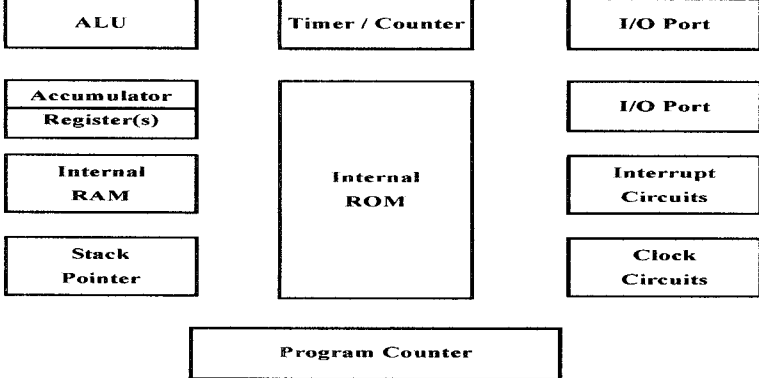22		2
23	 <p>Input and output wave forms</p>	2
24		3
25	<p>1) && 2) 3) !</p>	1 1 1
26	<p>Internet is a network of complex network. Long distance telephone and cable TV systems, To provide LAN connection, In college campus communication. (any two)</p>	1 2
Part -D		
27	<p>i) Voltage across $R_2 = V_2 = \left[\frac{R_2}{R_1 + R_2} \right] V_{CC} = \left[\frac{5K}{45K + 5K} \right] 20 = 2V$</p> <p>ii) $I_E = \left[\frac{V_2 - V_{BE}}{R_E} \right] = \frac{2 - 0.7}{1 \times 10^3} = 1.3mA$</p> <p>iii) $Z_{in\ base} = \beta r_e' = 100 \times \left[\frac{26mV}{1.3mA} \right] = 2k\ \Omega$</p> <p>iv) $Z_{in} = R_1 R_2 Z_{in\ base} = 45k 5k 2k = \dots\dots\dots = 1.38k\ \Omega$</p> <p>v) $Z_o = R_c R_L = 10k 10k = \dots\dots\dots = 5k\ \Omega$</p>	1 1 1 1 1

23	$V_{o1} = \left(\frac{-R_f}{R_1} \right) V_1$	1
	= = -600mV	1
	$V_o = - \left(\frac{R_f}{R_1} V_{o1} + \frac{R_f}{R_2} V_2 \right)$	1
	= = -4V (substitution and simplification)	2

29	$f = \frac{1}{2\pi\sqrt{L_T C}}$ where $L_T = L_1 + L_2$	1
	Substituting the value of f and C and simplifying for $L_T = 11.25\text{mH}$	3
	$L_2 = L_T - L_1 = 10.25\text{mH}$	1


30	i) Carrier frequency = $f_c = 6 \times 10^8 / 2\pi = 95.54\text{MHz}$.	1
	ii) Modulating frequency = $f_m = 1250 / 2\pi = 199\text{Hz}$.	1
	iii) Modulation index = $m_f = 5$	1
	iv) Maximum deviation = $\delta = m_f \times f_m = 995\text{Hz}$	1
	v) Carrier swing = $2\delta = 1990\text{Hz}$	1

31		<p>K-Map</p> <p>Entering 0s, 1s and x</p> <p>Proper grouping</p> <p>Boolean expression for Y</p> <p>NAND gate equivalent circuit</p>	1
			1
			1
			1
			1
			1

II	Comparison of CB, CC and CE amplifiers.			
32	Amplifier parameter	Types of Amplifiers		
		CB	CC	CE
	Current gain	Less than 1	Highest(1+β)	High β
	Voltage gain	Moderate	Less than 1	High
	Power Gain	Moderate	Moderate	Highest
	Phase Shift	0°	0°	180°
	Input impedance	Low	High	Moderate
	Output impedance	High	Low	Moderate
	Bandwidth	Wide	Wide	Narrow
		(any five)	5	

33

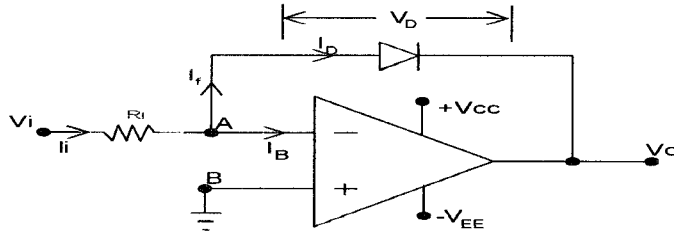A circuit whose output is proportional to logarithm of input.




Derivation.....

Final equation $V_o \propto \log_e(V_i)$

1
1
2
1

34

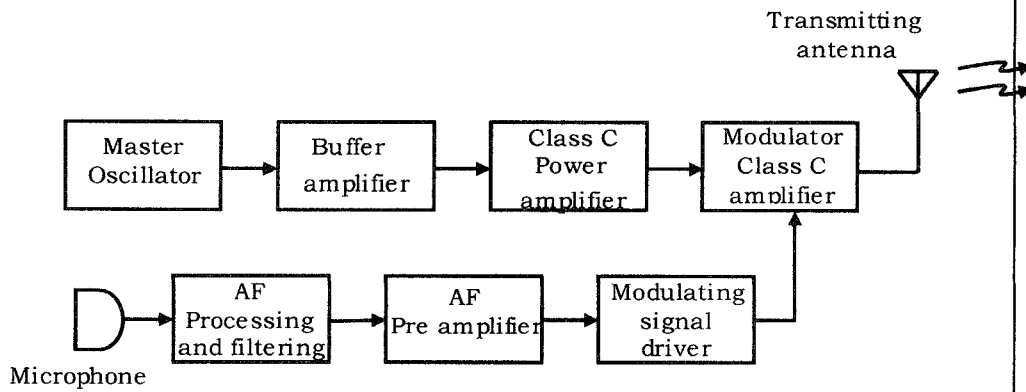


Block diagram of high level AM transmitter.

Block diagram with labelling

Working

3
2

35

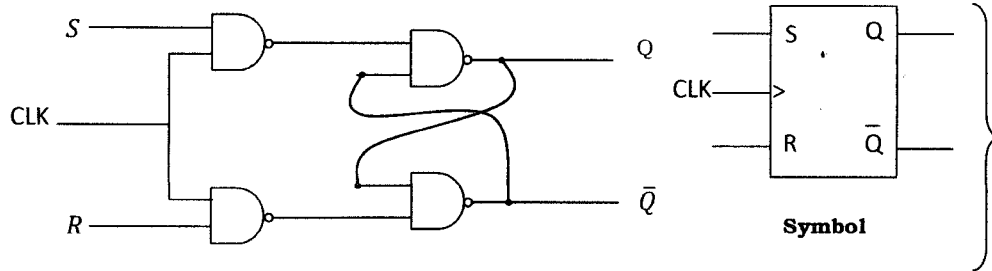

Clocked SR flip flop

Inputs			Outputs		Comment
CLK	S	R	Q_n	\bar{Q}_n	
1	0	0	Q_{n-1}	\bar{Q}_{n-1}	HOLD
1	1	0	1	0	SET
1	0	1	0	1	RESET
1	1	1	?	?	INVALID
0	X	X	Q_{n-1}	\bar{Q}_{n-1}	HOLD

Truth table

Note: X = any input state

Working

1
2
2

35	MOV A, #45H MOV R ₀ , #5EH ADD A, R ₀ MOV R ₁ , A 45H = 0100 0101 5EH = 0101 1110 <hr/> Content of R ₁ = 1010 0011 = A3H	1 1 1 1 1
37	<pre>#include<stdio.h> Void main() { int x,y,z,sum,avg; printf("enter the values of x,y,z"); scanf("%d%d%d", &x,&y,&z); sum=(x+y+z); avg= sum/3.0; printf("sum =%2d", sum); printf("avg = %2d", avg); }</pre> <p>Enter the values of x=5, y=6, z=7 sum = 18 avg=6</p>	1 1 1 1 1 1
- END -		